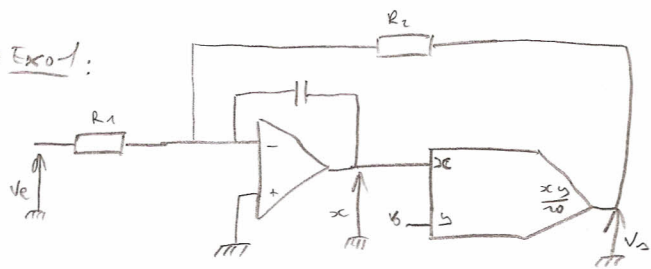


• Exo 1 :



$$Z_c = \frac{1}{j\omega C}$$

$$V_o = \alpha V_o \Rightarrow \alpha = \frac{V_o \cdot 10}{V_o}$$

$$V^- = \frac{V_o}{R_2} + \frac{\alpha V_o}{Z_c} + \frac{V_o}{R_1}$$

$$\frac{1}{R_1} + \frac{1}{Z_c} + \frac{1}{R_2}$$

$V^+ = 0$

on en déduit: $V_e Z_c R_2 + \alpha R_1 R_2 + V_o Z_c R_1 = 0$

$$V_e Z_c R_2 + \frac{V_o \cdot 10 R_1 R_2}{V_e} + V_o Z_c R_1 = 0$$

$$V_o \left(\frac{10 R_1 R_2}{V_o} + Z_c R_1 \right) = - R_2 Z_c V_e$$

$$\boxed{\frac{V_o}{V_e} = \frac{-R_2 Z_c}{Z_c R_1 + \frac{10 R_1 R_2}{V_o}}}$$

$$\frac{V_o}{V_e} = \frac{-R_2}{R_1 + \frac{10 R_1 R_2}{V_o Z_c}} = -\frac{R_2}{R_1} \times \frac{1}{1 + \frac{10 R_2}{V_o Z_c}}$$


$$\Rightarrow \frac{V_o}{V_e} = -\frac{R_2}{R_1} \times \frac{1}{1 + j \frac{10 R_2 C \omega}{V_o}}$$

$$\Rightarrow H(\omega) = \frac{H_0}{1 + j \frac{\omega}{\omega_0}} ; H(0) = -\frac{R_2}{R_1}$$

$$\omega_0 = \frac{V_o}{10 R_2 C}$$

Filtre passe bas

• Exo 2 :

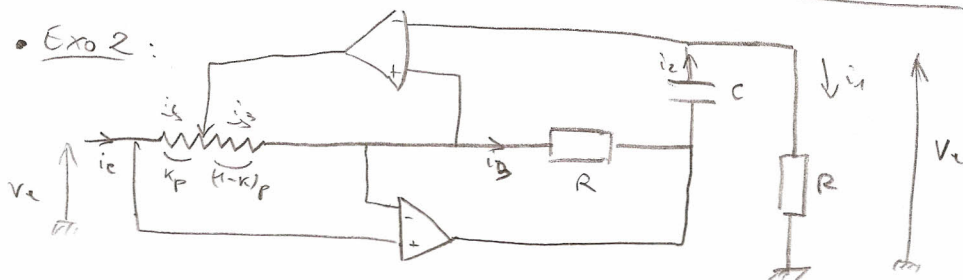

$$V_e = R i_4$$

$$i_4 = i_e$$

$$R i_2 + \frac{i_2}{C} = 0$$

$$i_2 = -R C i_3$$

$$k i_4 + (1-k) i_3 = 0$$


$$i_4 = -\frac{1-k}{k} i_3 \text{ or } i_4 = i_e$$

$$i_2 = -R C i_3 \text{ or } i_3 = -\frac{k}{1-k} i_4$$

$$i_2 = R C k \times \frac{k}{1-k} i_4 \text{ or } i_4 = i_e \text{ or } i_2 = i_4 \text{ or } i_2 = \frac{V_e}{R}$$

$$\Rightarrow \frac{V_e}{R} = R C k \frac{k}{1-k} i_e \Rightarrow \boxed{Z_c = \frac{V_e}{i_e} = \frac{k R^2 C}{1-k}}$$

• Exo 3:

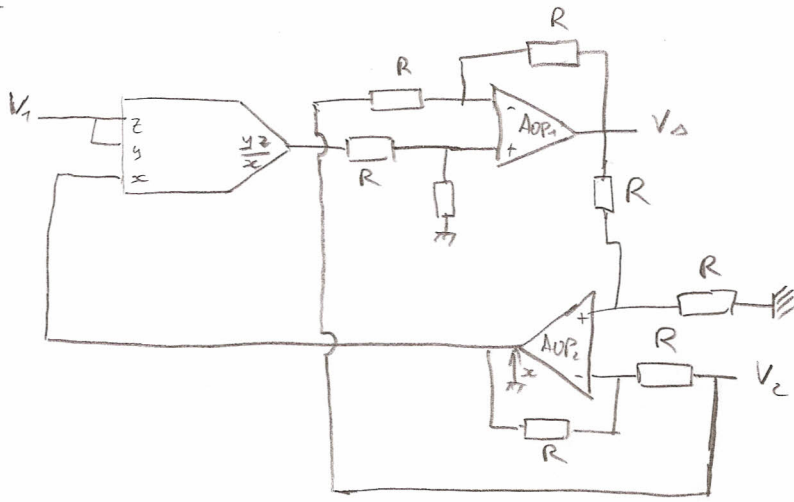

• AOP2: $V^+ = \frac{V_2}{2}$

$$V^- = \frac{\frac{x}{R} + \frac{V_2}{R}}{\frac{1}{R} + \frac{1}{R}} = \frac{x + V_2}{2}$$

$V^+ = V^-$

$$\Rightarrow \frac{x + V_2}{2} = \frac{V_2}{2} \Rightarrow \boxed{x = V_2 - V_2}$$

• AOP1: $V^+ = \frac{V_1^2}{2x}$
 $V^- = \frac{V_2 + V_2}{2}$

$V^- = V^+$
 $\Rightarrow \frac{V_1^2}{2x} = \frac{V_2 + V_2}{2}$

$\Rightarrow \frac{V_1^2}{x} = V_2 + V_2$


$\Rightarrow V_1^2 = (V_2 + V_2)(V_2 - V_2)$

$\Rightarrow V_1^2 = V_2^2 - V_2^2$

$\Rightarrow \boxed{V_2 = \sqrt{V_1^2 + V_2^2}}$

\Rightarrow on calcule le module.

• Exo 4:

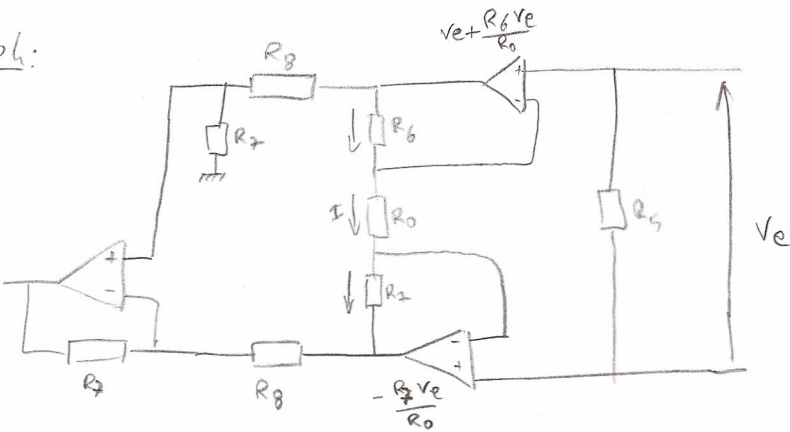

$I = \frac{V_e}{R_0}$

$V^+ = \frac{R_7}{R_7 + R_8} \left(V_e + \frac{R_6 V_e}{R_0} \right) = \frac{R_7}{R_7 + R_8} V_e \left(1 + \frac{R_6}{R_0} \right)$

$V^- = \frac{\frac{V_2}{R_7} - \frac{R_7 V_e}{R_0 R_0}}{\frac{1}{R_7} + \frac{1}{R_8}}$

$\Rightarrow V^- = \frac{V_2 R_8 - \frac{R_7^2}{R_0} V_e}{R_7 + R_8}$

$V^+ = V^- \Rightarrow R_7 V_e \left(1 + \frac{R_6}{R_0} \right) + \frac{R_7^2}{R_0} V_e = R_8 V_2$

$\Rightarrow \frac{R_7}{R_7 + R_8} V_e \left(1 + \frac{R_6}{R_0} \right) = \frac{V_2 R_8 - \frac{R_7^2}{R_0} V_e}{R_7 + R_8}$

$\Rightarrow V_2 = \left[\frac{R_7}{R_8} \left(1 + \frac{R_6}{R_0} \right) + \frac{R_7^2}{R_0 R_8} \right] V_e$

si $R_6 = R_7 = R_8 = R$

$\Rightarrow \boxed{V_2 = \left(1 + \frac{2R}{R_0} \right) V_e}$